

Plan

Synchronous Circuit

- Combinational Circuit
- Sequential Circuit
- Digital Watch

Binary Algebra

- Boolean Algebra
- Binary z- Transform
- 2-adic Numbers

Electronic Circuit

- Transistor
- Silicon Process
- MOS Structures

Silicon Arithmetic

- Counters
- Adders
- Multipliers

Universal Machines

- Microprocessor
- Programmable Logic
- Computable Functions

Digital Physics

- CCD Camera
- Radiation Detector
- Heat Equation






Information Theory

- Shannon's Theory
- Entropy Coding
- Error Coding

Audio & Video

- Digital Audio
- JPEG Compression
- Half Toning





Switch

     




Mémoire d'ordinateur, 195*




Transistor

    

Planar FET

 
 
 


Digital Transistor


 


cMOS Transistor

   - * **Blocked:** $V_{gd} < V_{th}$ $I_{sd} = 0$
- * **Resistive:** $V_{gd} - V_{th} > V_{sd}$ $I_{sd} = c_n (V_{gd} - V_{th})^2$
- * **Saturated:** $V_{gd} - V_{th} < V_{sd}$ $I_{sd} = c_n (V_{gd} - V_{th})^2 / 2$





Invert

  


Multiplex



Multiplexeur

  


cMOS MUX

 



cMOS XOR

  

cMOS LUT2


 


Custom Full Adder



 
 


Digital Time & Register





 
 
$$clk(t) = \sum_{n \in \mathbb{N}} \delta(t - n)$$




Masks

    


MOS Process

     
 


Silicon Foundry




 


Floor Plan

 


  


Delays: RC Model

    



Power

 




Clock

 

Fast Counter

  


Shrink Laws

   


Gains

- Size
- Speed
- Power
- Reliability
- Cost


Shrink

 


Chip History

 


Moore's Laws

 


Memories

 

Processors

 

 


Aluminum
conductors
(5 levels)

Oxide
dielectric

Tungsten
Plugs

The device

0.1 μm

 


Copper
conductors
(8 levels)

Low-K
dielectric



Copper
Plugs

The device

Internet

 

cMOS End Point

 
 


Limits


- Physics
- Technology
- Economics

2015?


Memory

  

2^N ways MUX


 


$$|mux(2^N)| = N2^N$$

 



$$|mux(2^N)| = \max \left\{ (2^N - 1) |mux|, N2^N |wire| \right\}$$

Bus

  


2^N ways deMUX


$$|demux(2^N)| = N2^N$$

  


ROM

 


ROM: Full Adder

 

Dual Port Memory

 


Single Port Memory

 

sRAM

6 transistors/bit

5 transistors/bit

 

dRAM

1 transistor/bit

1/2 transistor/bit

