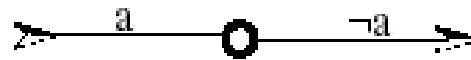


# Boolean Gates


NOT



$$a = \{N : a_N = 1\} \quad b = \{N : b_N = 1\} \quad c = \{N : c_N = 1\}$$


$$c = \neg a$$
$$c_N = 1 - a_N$$

AND

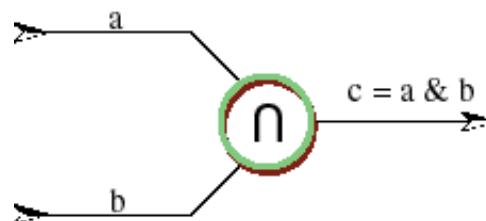


$$c = a \cap b$$
$$c_N = a_N \cap b_N = a_N b_N$$

OR

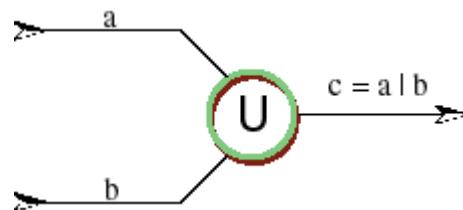

$$c = a \cup b$$
$$c_N = a_N \cup b_N = a_N + b_N - a_N b_N$$

XOR

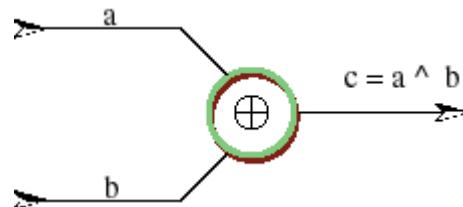

$$c = a \oplus b$$
$$c_N = a_N \oplus b_N = a_N + b_N - 2a_N b_N$$

# Multiplexer


$$\langle x, \neg mux \rangle$$

$$\neg x = mux(x, 0, \bar{0})$$

$$\langle 0, \bar{0}, x, mux \rangle$$

$$x \cap y = mux(x, y, x)$$

$$x \cup y = mux(x, x, y)$$

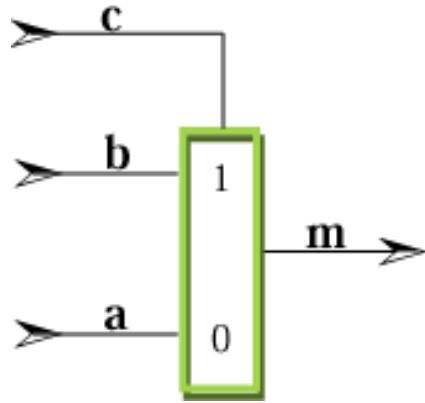

$$m = mux(c, b, a)$$

$$m = c?b:a$$

$$c_N = 0 : m_N = a_N$$

$$c_N = 1 : m_N = b_N$$

$$m = (c \cap b) \uplus (\neg c \cap a)$$

$$m_N = c_N b_N + (1 - c_N) a_N$$


$$m = a \oplus (c \cap (a \oplus b))$$

## Shannon Decomposition

$$\begin{aligned}
 f(x_1 x_2 \cdots x_i) &= (\neg x_1 \cap f(0 x_2 \cdots x_i)) \cup (x_1 \cap f(1 x_2 \cdots x_i)) \\
 &= mux(x_1, f(1 x_2 \cdots x_i), f(0 x_2 \cdots x_i)) \\
 &= (1 - x_1) f(0 x_2 \cdots x_i) + x_1 f(1 x_2 \cdots x_i)
 \end{aligned}$$

# Full Adder

## Icon

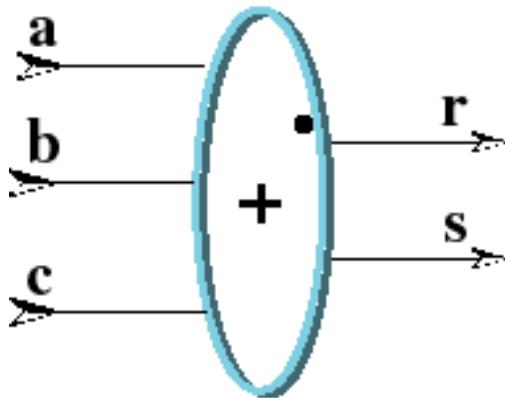



## Function

$$a_N + b_N + c_N = s_N + 2r_N$$

## Specification

$$s_N = a_N \oplus b_N \oplus c_N$$
$$r_N = a_N b_N \oplus b_N c_N \oplus c_N a_N$$

## Implementations

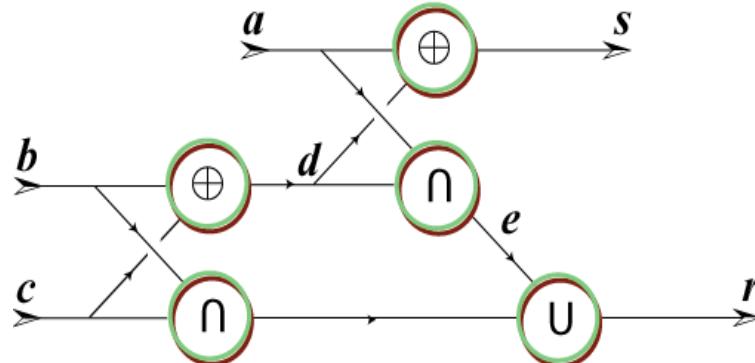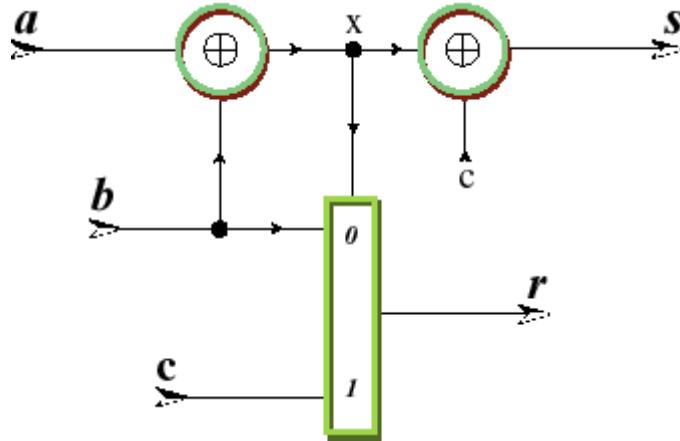

# Boolean Basis

$$<0, x, \neg, \cap, \cup, \oplus>$$
$$<x, \neg, \cap, \cup>$$
$$\bar{0} \notin <0, x, \cap, \cup, \oplus>$$
$$<\bar{0}, x, \cap, \oplus>$$
$$<x, \overline{\cap}>$$

$$0 = x \oplus x$$


$$a \oplus b = (a \cap \neg b) \cup (\neg a \cap b)$$

$$\bar{0} = \neg 0 = -1 = (1) = \frac{1}{1-z}$$

$$\begin{aligned}\neg x &= \bar{0} \oplus x \\ a \cup b &= a \oplus b \oplus (a \cap b)\end{aligned}$$

$$\begin{aligned}\neg a &= a \overline{\cap} a \\ a \cup b &= (\neg a) \overline{\cap} (\neg b) \\ a \cap b &= \neg(a \overline{\cap} b)\end{aligned}$$

# Net-list

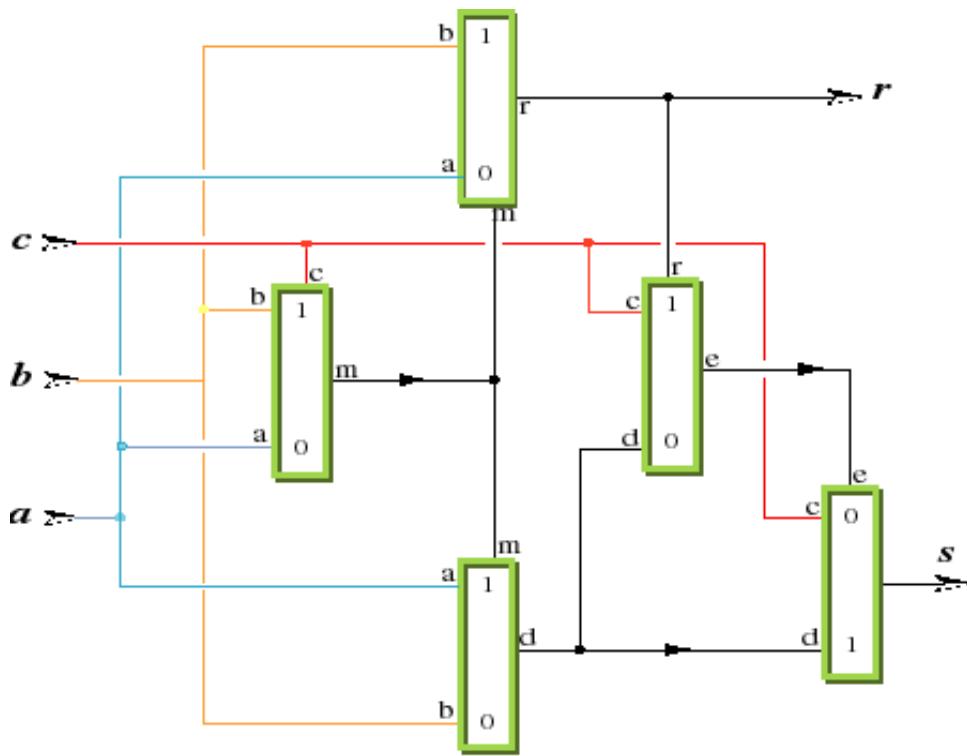

$$s = \text{mux}(e, d, c)$$

$$r = \text{mux}(m, b, a)$$

$$m = \text{mux}(c, b, a)$$

$$d = \text{mux}(m, a, b)$$

$$e = \text{mux}(r, c, d)$$

$$m = \text{mux}(c, b, a);$$



$$d = \text{mux}(m, a, b); \quad r = \text{mux}(m, b, a);$$

$$e = \text{mux}(r, c, d);$$

$$s = \text{mux}(e, d, c);$$


## Topological Sort

# Physical Simulation

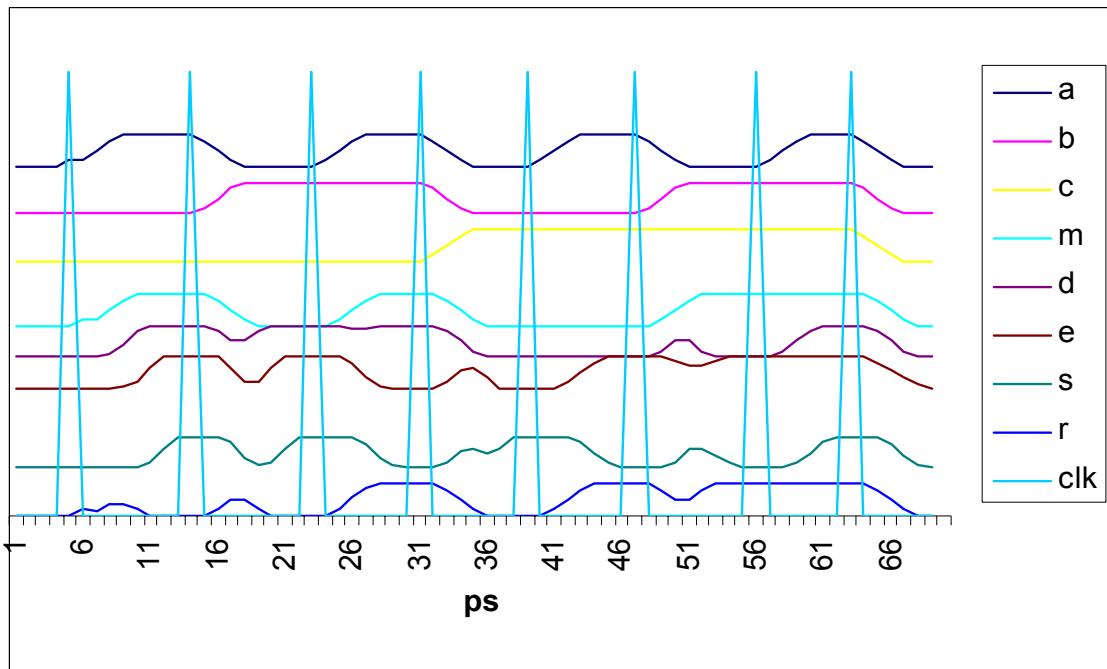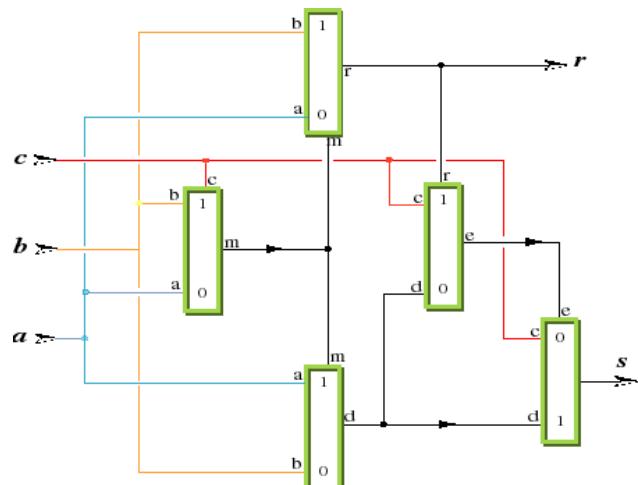

ps	a	b	c	m	d	e	s	r
0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0
2	0	0	0	0	0	0	0	0
3	0	0	0	0	0	0	0	0
4	0	0	0	0	0	0	0	0
5	0	0	0	0	0	0	0	0
6	1	0	0	0	0	0	0	0
7	1	0	0	1	0	0	0	0
8	1	0	0	1	0	0	0	0
9	1	0	0	1	1	0	0	0
10	1	0	0	1	1	1	0	0
11	1	0	0	1	1	1	1	0
12	1	0	0	1	1	1	1	0
13	1	0	0	1	1	1	1	0
14	1	0	0	1	1	1	1	0
15	1	1	0	1	1	1	1	0
16	0	1	0	1	1	1	1	1
17	0	1	0	0	1	0	0	1
18	0	1	0	0	1	0	0	0
19	0	1	0	0	1	1	0	0
20	0	1	0	0	1	1	1	0
21	0	1	0	0	1	1	1	0
22	0	1	0	0	1	1	1	0
23	0	1	0	0	1	1	1	0
25	1	1	0	0	1	1	1	0
26	1	1	0	1	1	1	1	1
27	1	1	0	1	1	0	1	1
28	1	1	0	1	1	0	0	1
29	1	1	0	1	1	0	0	1
30	1	1	0	1	1	0	0	1
31	1	1	0	1	1	0	0	1

# Logical Simulation

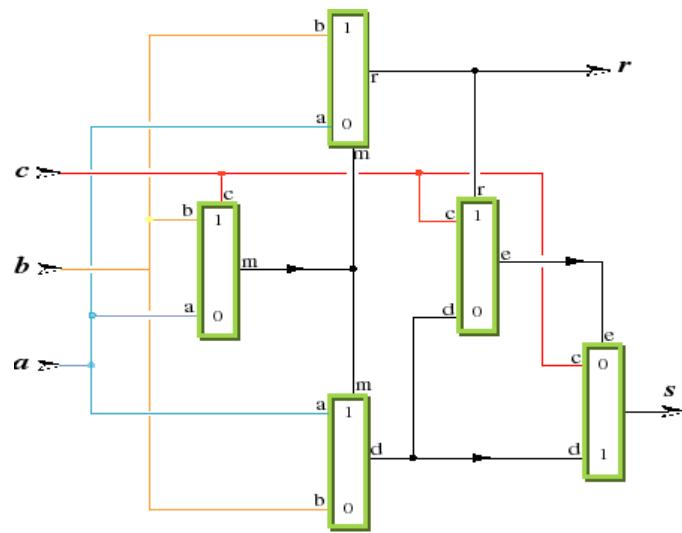

## Topological Sort

$$m = \text{mux}(c, b, a)$$

$$r = \text{mux}(m, b, a), d = \text{mux}(m, a, b)$$


$$e = \text{mux}(r, c, d)$$

$$s = \text{mux}(e, d, c)$$

<b>a</b>	<b>b</b>	<b>c</b>	<b>s</b>	<b>r</b>	<b>d</b>	<b>m</b>	<b>e</b>	<b><math>a+b+c</math></b>	<b><math>s+2r</math></b>
0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	1	1	1	1	1
0	1	0	1	0	1	0	1	1	1
1	1	0	0	1	1	1	0	2	2
0	0	1	1	0	0	0	0	1	1
1	0	1	0	1	0	0	1	2	2
0	1	1	0	1	0	1	1	2	2
1	1	1	1	1	1	1	1	3	3
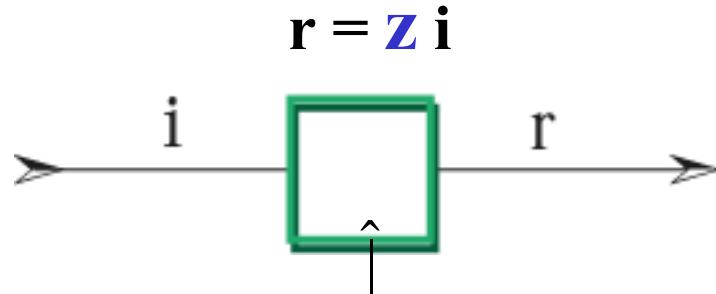
# Synchronous Register

$$i = \sum i_N 2^N$$
$$r = \sum r_N 2^N$$




$$r_{N+1} = i_N$$
$$r_0 = 0$$

Clock is implicit:

$$t = \sum_{n \in \mathbb{N}} \delta(t - n)$$

$$r = 2i$$

All registers share the same clock.

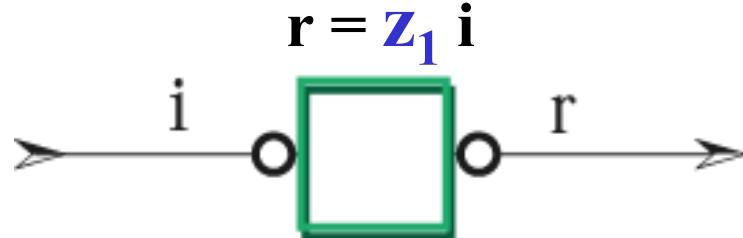

$$r = 1 + 2i$$

$$r_{N+1} = i_N$$
$$r_0 = 1$$

# Feedback

**Problem:**  $\text{bad} = \neg \text{bad}$

$$\text{bad}_0 = 1 - \text{bad}_0$$

$$\text{bad}_0 = \frac{1}{2} \notin \{0,1\}$$




**No problem:**  $\text{tog} = z \neg \text{tog}$

$$\text{tog}_0 = 0$$

$$\text{tog}_{2N} = 0$$

$$\text{tog}_{N+1} = 1 - \text{tog}_N$$

$$\text{tog}_{2N+1} = 1$$

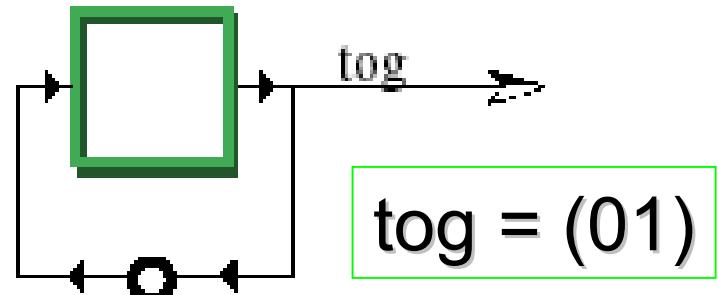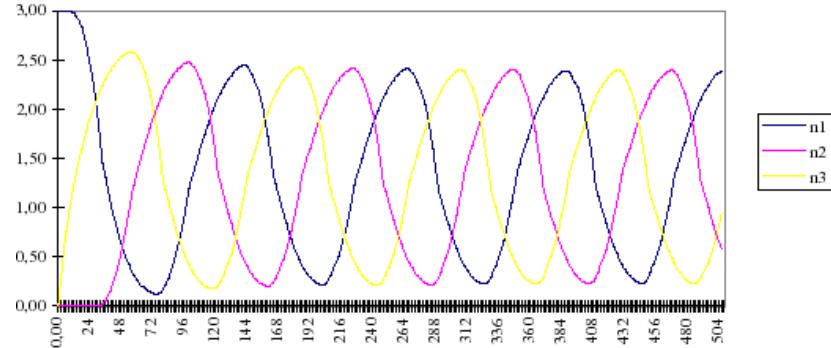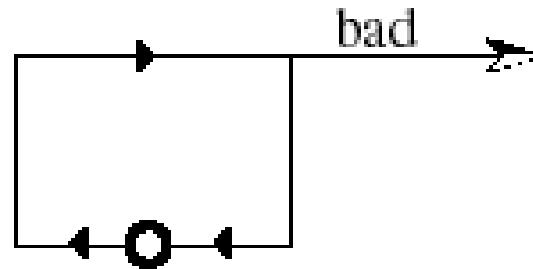

**Solutions:**

1. **No** combinational feedback
2. **Stable** combinational feedback

# Sequential Circuit


## Schema

$$cm2(i) = (s, c)$$

Net-list

$$\{ s = z(i \oplus s) \}$$

$$c = i \cap s \}$$

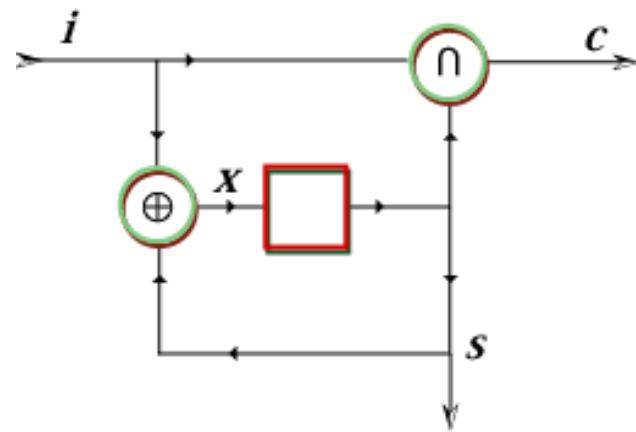

## Infinite Boolean System

$$s_0 = 0$$

$$s_1 = x_0$$

$$s_N = x_{N-1}$$

$$x_0 = i_0$$

$$x_1 = i_1 \oplus s_1$$

...

$$x_N = i_N \oplus s_N$$


...

$$c_0 = 0$$

$$c_1 = i_1 \cap s_1$$

$$c_N = i_N \cap s_N$$

# Binary Counter

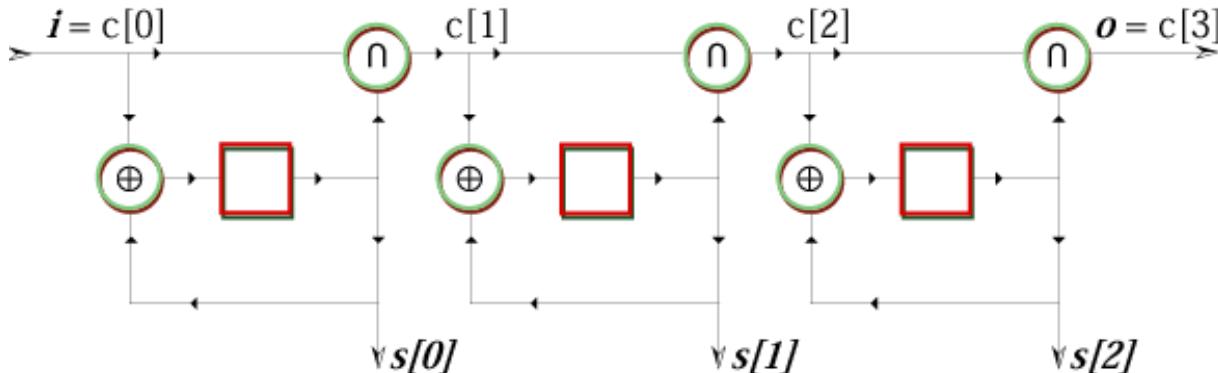

```
// Binary n bit counter
fun Counter(n:int)(incr:net)= (s:net[n], ovfl:net) {
```

```
    c[0]=incr; // carry in
    ovfl=c[n]; // carry out
    for (k<n) (s[k] , c[k+1] ) = cm2(c[k]); }
```

```
// Counter modulo 2
```

```
fun cm2 (incr:net)= (s:net, ovfl:net) {
    s = reg(incr ^ s);
    ovfl = incr & s; }
```