

Digital Synchronous System

Binary values: $\forall t \in \mathbb{R} \geq 0 : v_t \in \mathbb{B} = \{0, 1\}$

Synchronous: $\forall t \in \mathbb{R} : v_t = v_n, n = \lfloor t \rfloor$

Digital Signal:

$$v_t = \int_{t-1}^t v'_x dx$$
$$v'_t = \sum_{n \in \mathbb{N}} v_n \delta(t - n)$$

Binary sequence: $(v_{\mathbb{N}}) = v_0 v_1 v_2 \dots$

Digital Function

$$\mathbb{D} \rightarrow \mathbb{D}$$

Digital Number $d = \llbracket d_0 \dots \{d\} d(z) d(2) \rrbracket$


1. *Continuous*: each output depends upon finitely many input.
2. *Computable*: presented by a finite program.
3. *Causal*: present output depends upon past input.
4. *Sequential*: causal + finite \Leftrightarrow circuit function.

Counter Modulo 2

$$s = Z x$$

$$x = i \oplus s$$

$$c = i \cap s$$

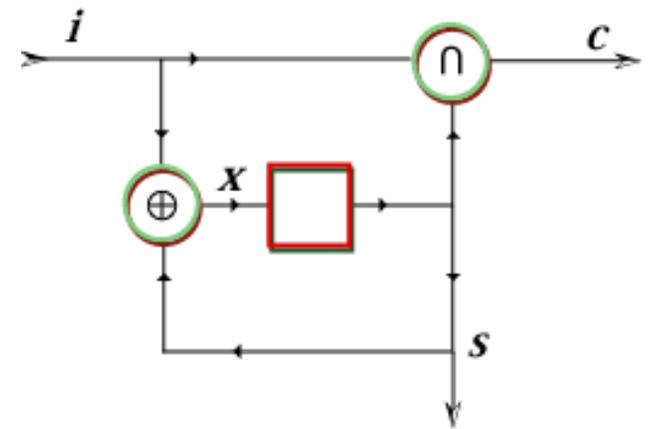

$$s_0 = 0$$

$$s_N = x_{N-1}$$

$$x_0 = i_0$$

$$x_N = i_N \oplus s_N$$

$$c_0 = 0$$

$$c_N = i_N s_N$$

Causal

$$s_N = g_N(i_0 \cdots i_{N-1})$$


$$c_N = h_{N+1}(i_0 \cdots i_N)$$

Finite

$$s_{N+1} = f_s(i_N, s_N)$$

$$c_N = f_y(i_N, s_N)$$

Sequential Function

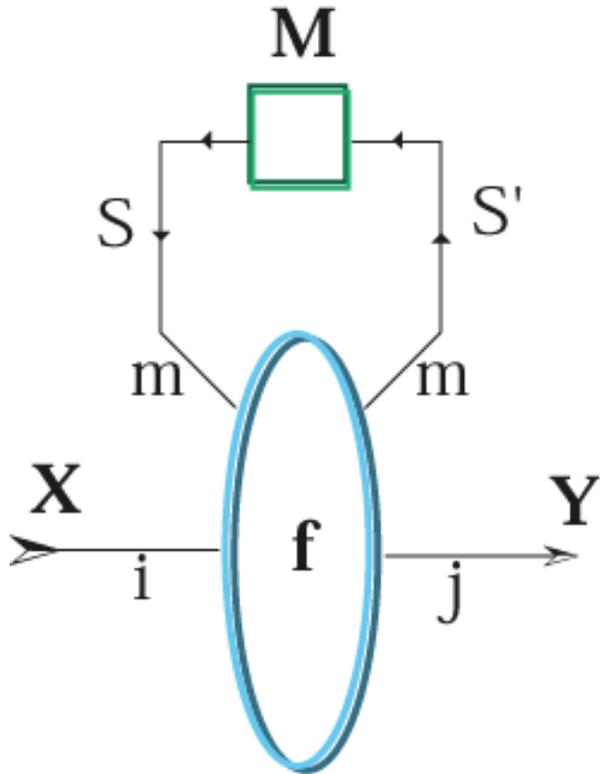

Causal

$$y_N = f_N(x_0 \cdots x_N)$$

$\forall n \in \mathbb{N}$:

$$f_n \in \mathbb{B}^{i(n+1)} \rightarrow \mathbb{B}^j$$

Finite Memory

$$s_{N+1} = f^s(x_N, s_N)$$

$$f^s \in \mathbb{B}^{i+m} \rightarrow \mathbb{B}^m$$

$$y_N = f_y(x_N, s_N)$$

$$f_y \in \mathbb{B}^{i+m} \rightarrow \mathbb{B}^j$$

State Encoding:


$$s_N = \sum_{1 \leq k \leq m} m_N[k] 2^{k-1}$$

Reachable States: rs

$$|regs| \geq \log_2 |rs|$$

$$|states| \leq 2^{|regs|}$$

CM 2

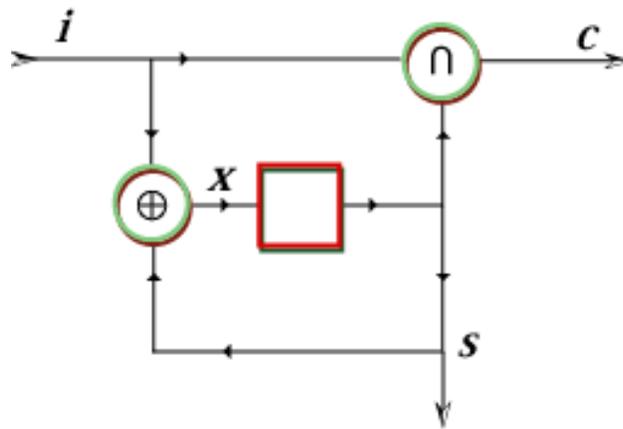

$$s = Z x$$

$$x = i \oplus s$$

$$c = i \cap s$$

$$s_N = 0$$

$$s_{N+1} = i_N \oplus s_N$$

$$c_N = i_N s_N$$

$$s_N = i_0 \oplus i_1 \oplus \dots \oplus i_{N-1}$$

$$s_N = \sum_{k < N} i_k \pmod{2}$$


$$s_N = 0$$

$$s_{N+1} = i_N + s_N - 2i_N s_N$$

$$c_N = i_N s_N$$


$$\sum_{k < N} i_k = s_N + 2 \sum_{k < N} c_k$$

Counter Modulo 8

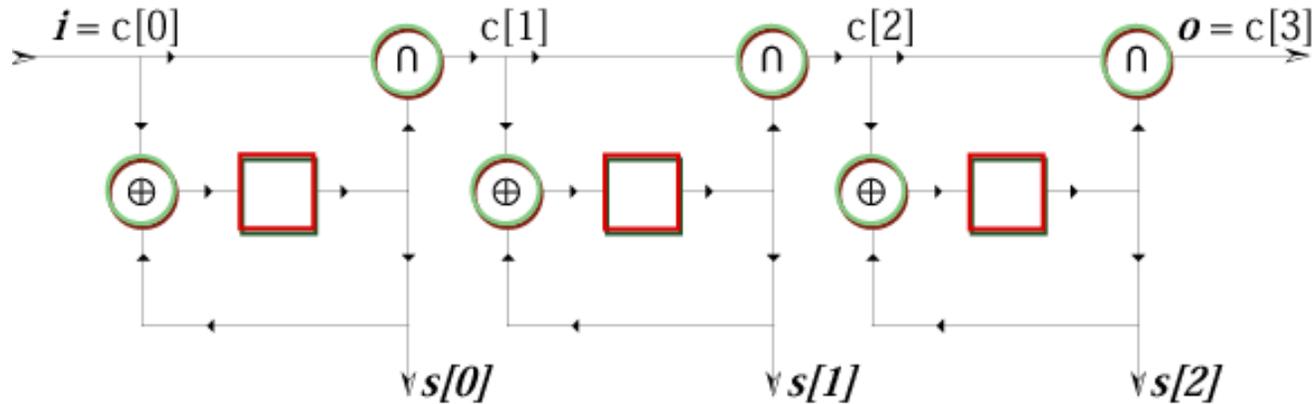

cycle	$i = c[0]$	$s[0]$	$s[1]$	$s[2]$	$c[1]$	$c[2]$	$x[0]$	$x[1]$	$x[2]$	o
0	1	0	0	0	0	0	1	0	0	0
1	1	1	0	0	1	0	0	1	0	0
2	1	0	1	0	0	0	1	1	0	0
3	1	1	1	0	1	1	0	0	1	0
4	1	0	0	1	0	0	1	0	1	0
5	1	1	0	1	1	0	0	1	1	0
6	1	0	1	1	0	0	1	1	1	0
7	1	1	1	1	1	1	0	0	0	1
8	1	0	0	0	0	0	1	0	0	0

Counter Modulo 8

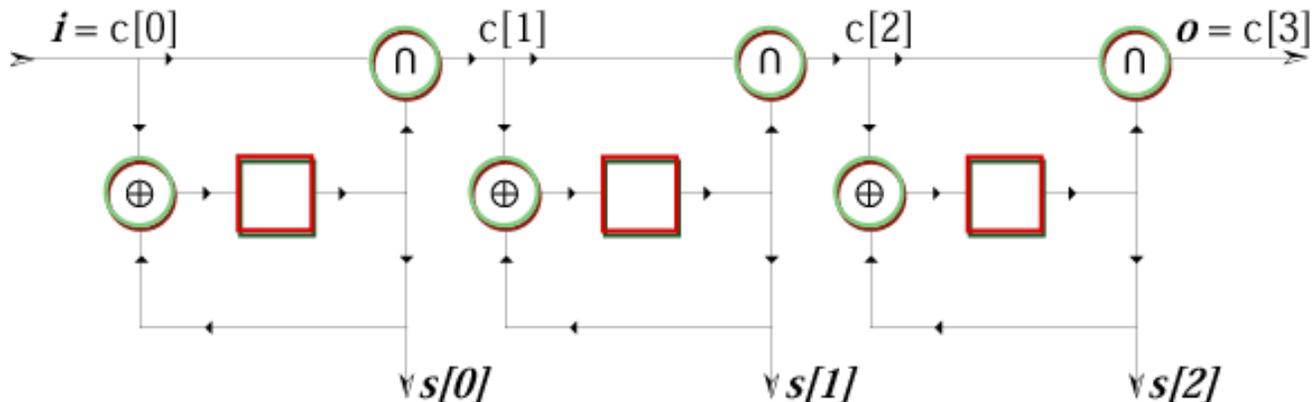

$$\sum_{k < N} c_k[0] = s_N[0] + 2 \sum_{k < N} c_k[1]$$

$$\sum_{k < N} c_k[1] = s_N[1] + 2 \sum_{k < N} c_k[2]$$

$$\sum_{k < N} c_k[2] = s_N[2] + 2 \sum_{k < N} c_k[3]$$

$$\sum_{k < N} c_k[0] = S_N + 8 \sum_{k < N} c_k[3]$$

$$S_N = s_N[0] + 2s_N[1] + 4s_N[2]$$